 



Application: Digital logic circuits

Logic and electric circuits



"in series"

P	Q	light
<i>closed</i>	<i>closed</i>	on
<i>closed</i>	<i>open</i>	off
<i>open</i>	<i>closed</i>	off
<i>open</i>	<i>open</i>	off

 


"in parallel"

Q	Q	light
<i>closed</i>	<i>closed</i>	on
<i>closed</i>	<i>open</i>	on
<i>open</i>	<i>closed</i>	on
<i>open</i>	<i>open</i>	off

Modern computers use **logic gates**


Basic logic gates

AND gate

 


P	Q	R
1	1	1
1	0	0
0	1	0
0	0	0

OR gate

 


P	Q	R
1	1	1
1	0	1
0	1	1
0	0	0

NOT gate

 

P	R
1	0
0	1

Rules for a combinatorial circuit

 


- Never combine two input wires.
- A single input wire can be split partway and used as input for two separate gates.
- An output wire can be used as input.
- *No output of a gate can eventually feed back into that gate.*


Determining output for a given circuit

Input signals: $P = 0$ and $Q = 1$

Boolean expression

 

 Input signals: $P = 1$, $Q = 1$ and $R = 1$




Constructing circuits for Boolean expressions



■ $(\neg P \wedge Q) \vee \neg Q$
2 1



 ■ $((P \wedge Q) \wedge (R \wedge S)) \wedge T$




Multi-input AND and OR gates

  



Designing a circuit for a given input/output table

Input			Output
P	Q	R	S
1	1	1	1
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	0
0	1	0	0
0	0	1	0
0	0	0	0

 

$$(P \wedge Q \wedge R) \vee (P \wedge \neg Q \wedge R) \vee (P \wedge Q \wedge \neg R)$$

disjunctive normal form (DNF)

  


$c = \text{high}$
 $e = \text{high}$



$b = \text{high}$
 $i = \text{high}$
 $c = \text{high}$
 $e = \text{high}$

Another example

Input			Output
P	Q	R	S
1	1	1	1
1	1	0	0
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	1
0	0	0	0

 


$$(P \wedge Q \wedge R) \vee (P \wedge \neg Q \wedge R) \vee \\ (\neg P \wedge Q \wedge R) \vee (\neg P \wedge \neg Q \wedge R)$$



Reopen the first case

Input			Output
P	Q	R	S
1	1	1	1
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	0
0	1	0	0
0	0	1	0
0	0	0	0

$$P \wedge (Q \vee R)$$

 

Circuit equivalence

  

- Two digital circuits are **equivalent** if they produce the same output given the same inputs.

Logical equivalence

Definition Two formulas P and Q are called **equivalent** if they have the same truth value under every possible interpretation. In other words, P and Q are equivalent if $I(P) = I(Q)$ for every interpretation I . This is denoted by

$$P \equiv Q.$$

Example:

$$(P \wedge Q \wedge R) \vee (P \wedge \neg Q \wedge R) \vee (P \wedge Q \wedge \neg R) \equiv P \wedge (Q \vee R)$$

Theorem The relation \equiv is an equivalence relation on \mathcal{P} .

Proof

- \equiv is reflexive, since, trivially, $I(P) = I(P)$ for every interpretation I .
- \equiv is transitive, since $P \equiv Q$ and $Q \equiv R$ implies $P \equiv R$.
- \equiv is symmetric, since $P \equiv Q$ implies $Q \equiv P$.

Simplifying propositional formulae

Exercises:

- $(P \Rightarrow Q) \equiv (\neg P \vee Q)$
- $\neg(P \Rightarrow Q) \equiv (P \wedge \neg Q)$
- $(P \Leftrightarrow Q) \equiv ((P \Rightarrow Q) \wedge (Q \Rightarrow P))$
- $(P \Leftrightarrow Q) \equiv (\neg P \Leftrightarrow \neg Q)$
- $(P \wedge (P \vee Q)) \equiv P$
- $\neg(P \vee (\neg P \wedge Q)) \equiv (\neg P \wedge \neg Q)$

Useful equivalences

The following equivalences can be checked by truth tables:

- Associative laws:

$$(P \vee (Q \vee R)) \equiv ((P \vee Q) \vee R),$$

$$(P \wedge (Q \wedge R)) \equiv ((P \wedge Q) \wedge R);$$

- Commutative laws:

$$(P \vee Q) \equiv (Q \vee P), \quad (P \wedge Q) \equiv (Q \wedge P);$$

- Identity laws:

$$(P \vee \perp) \equiv P, \quad (P \vee \top) \equiv \top, \quad (P \wedge \top) \equiv P, \quad (P \wedge \perp) \equiv \perp;$$

■ Distributive laws:

$$(P \wedge (Q \vee R)) \equiv ((P \wedge Q) \vee (P \wedge R))$$


$$(P \vee (Q \wedge R)) \equiv ((P \vee Q) \wedge (P \vee R));$$

■ Complement laws:

$$P \vee \neg P \equiv \top, \neg \top \equiv \perp, \neg \neg P \equiv P, P \wedge \neg P \equiv \perp, \neg \perp \equiv \top;$$

■ De Morgan's laws:
 
$$\neg(P \vee Q) \equiv (\neg P \wedge \neg Q), \neg(P \wedge Q) \equiv (\neg P \vee \neg Q).$$






Boolean functions of arity 2

P	Q	\perp	\wedge	$\neg(P \vee Q)$ $\neg(P \wedge Q)$	P	$\neg(Q \wedge P)$ $\neg(P \wedge Q)$	Q	$\neg(P \vee \neg Q)$ $P \vee \neg Q$	\vee
1	1	0	1	0	1	0	1	0	1
1	0	0	0	1	1	0	0	1	1
0	1	0	0	0	0	1	1	1	1
0	0	0	0	0	0	0	0	0	0


P	Q	$\neg(P \vee Q)$	$P \vee \neg Q$	$\neg Q$	$Q \vee \neg P$	$\neg P$	$P \vee Q$	$\neg(P \wedge Q)$	T
1	1	0	1	0	1	0	1	0	1
1	0	0	0	1	1	0	0	1	1
0	1	0	0	0	0	1	1	1	1
0	0	1	1	1	1	1	1	1	1

Logic gates




■ AND, OR, NOT

   

■ XOR

 

■ NAND, NOR, XNOR

   

Universality of NAND and NOR

- NAND (AKA Sheffer stroke)
- and NOR (AKA Pierce arrow)

$$P \mid Q = \neg(P \wedge Q)$$


$$P \downarrow Q = \neg(P \vee Q)$$

are universal:


$$\neg P \equiv P \mid P$$


 
$$P \vee Q \equiv (P \mid P) \mid (Q \mid Q)$$


 
$$P \wedge Q \equiv (P \mid Q) \mid (P \mid Q)$$






A bit on sequential circuits


Rules for a sequential circuit

- Never combine two input wires.
- A single input wire can be split partway and used as input for two separate gates.
- An output wire can be used as input.
- An output of a gate **can** eventually feed back into that gate.


What happens here?

   

Same behaviour

 

is same as

 

NOR gates

Set/Reset flip-flop circuit

AKA latch

